

Note 1: You must **explain all your calculations clearly** to get full credit.

Note 2: This assessment will be graded out of 40 marks. 90% of the grade for this coursework (36/40) will be assigned for a **correct, well-argued calculation**. Another 10% (4/40) will be awarded at the grader's discretion for **clarity and presentation** of your solution.

Note 3: Due by **midday on Monday February 6th 2023**. Please submit via the Turnitin dropbox link provided in Blackboard.

Coursework background: Let $N > 1$ be a positive integer. Given an N -node graph viewed as a resistive electric circuit with all edges having unit conductance, the resistance matrix \mathbf{R} is defined as the matrix with components R_{ij} given by the effective resistance between node i (set to unit voltage) and node j (grounded) with all diagonal elements taken to vanish, i.e. $R_{ii} = 0$. Recall that the effective resistance is just the reciprocal of the effective conductance C_{eff} introduced in lectures.

The *total effective resistance* of the graph is defined in terms of this resistance matrix as

$$R^{(\text{total})} = \sum_{i < j} R_{ij}. \quad (1)$$

Let the orthonormal (i.e., unit length and mutually orthogonal) eigenvectors and corresponding eigenvalues of the N -by- N graph Laplacian \mathbf{K} be denoted by

$$\{\mathbf{e}_k | k = 1, \dots, N\}, \quad \{\lambda_k | k = 1, \dots, N\},$$

where we take

$$\mathbf{e}_1 = \frac{1}{\sqrt{N}} \begin{pmatrix} 1 \\ 1 \\ \vdots \\ \vdots \\ 1 \end{pmatrix}, \quad \lambda_1 = 0$$

and where we denote the elements of \mathbf{e}_k for $k = 2, \dots, N$ as

$$\mathbf{e}_k = \begin{pmatrix} e_{k1} \\ e_{k2} \\ \vdots \\ \vdots \\ e_{kN} \end{pmatrix}, \quad k = 2, \dots, N.$$

The following two formulas can be established relating the elements of the resistance matrix and the total effective resistance to the eigenvectors/eigenvalues of \mathbf{K} :

$$R_{ij} = \sum_{k=2}^N \frac{1}{\lambda_k} (e_{ki} - e_{kj})^2 \quad (2)$$

and

$$R^{(\text{total})} = N \sum_{k=2}^N \frac{1}{\lambda_k}. \quad (3)$$

Coursework exercise: Consider the 4-node graph shown in Figure 1:

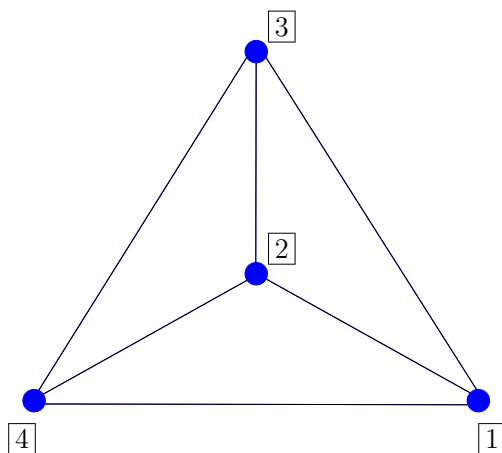


Figure 1: A 4-node graph viewed as an electric circuit.

- Using the node labelling given in the figure, find the resistance matrix \mathbf{R} for this graph.
- Hence, using your results from part (a), compute R^{total} for this graph using formula (1).
- Find the eigenvalues $\{\lambda_k | k = 1, \dots, 4\}$ and orthonormal eigenvectors $\{\mathbf{e}_k | k = 1, \dots, 4\}$ of the graph Laplacian \mathbf{K} .
- Use the results of parts (a) and (c) to verify formula (2).
- Use the results of parts (b) and (c) to verify formula (3).
- Prove formula (2). *Hint:* consider using the eigenvectors as a basis.
[Note: you are not required to prove formula (3)].